



Computer Fundamentals

Lecture 9 : Logic & Control - Part III

Objectives



- ❑ After completing this module you will be able to:
 - Understand Combinational Circuits
 - ❑ Decoder, Multiplexer, Comparator, Arithmetic Circuits
 - Understand Sequential Circuits
 - ❑ SR, JK, D, T Flip-flops
 - Understand the arrangement of the ALU

Lecture Outline

- ❑ Integrated Circuits
- ❑ Combinational Circuits
 - Half adder & Full adder
 - The use of the Decoder, Multiplexer, De-multiplexer.
 - Enable input of a digital device.
- ❑ Sequential Circuits (Fundamental Building Blocks of Memory)
 - Introduction to SR Latch (Level triggered Flip-flops).
 - Concept of the Flip-flop (Edge Triggered Flip-flops).

Integrated Circuits (ICs)

  - ❑ An Integrated Circuit is a small silicon semiconductor crystal(chip), containing the electronic components for digital gates.
- ❑ Various gates are interconnected inside the chip to form the required circuits.
- ❑ Chip is mounted in a ceramic or plastic container and connections are welded by thin gold wires to the external pins to form the integrated circuit.



Integrated Circuits (ICs)

- ❑ The IC pins provide access to the input and output terminals of individual gates as well as power supply to the whole device.

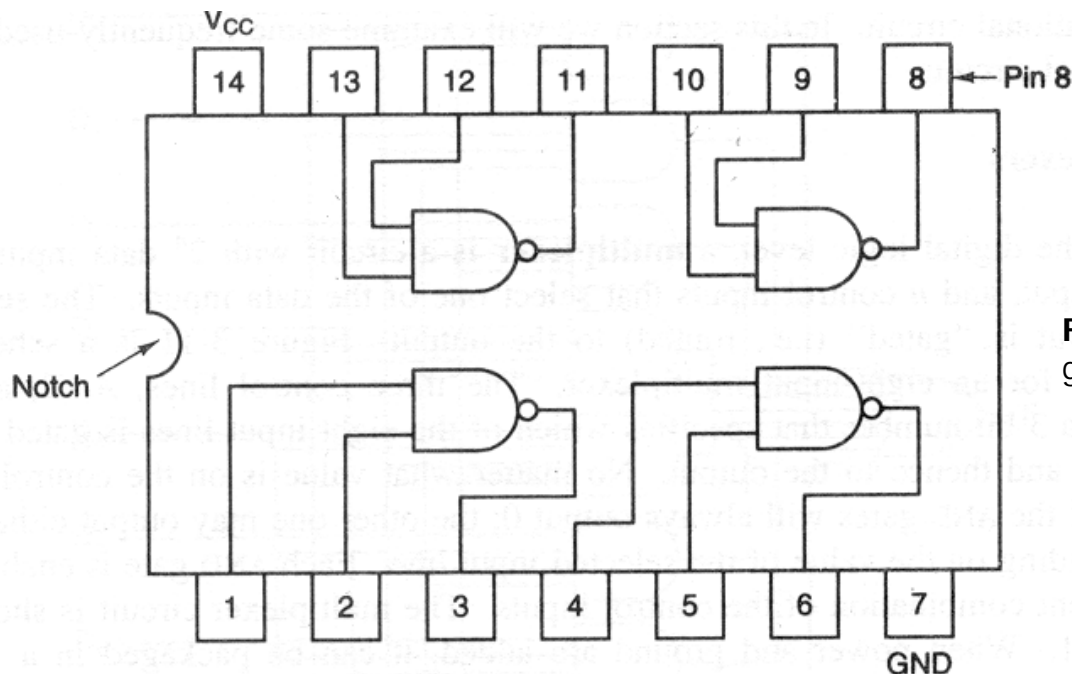


Figure 4-17. An SSI chip containing four gates.

Integrated Circuits (Contd.)

- ❑ ICs are roughly classified based on the number of gates they contain:
 - ❑ **SSI (Small Scale Integrated) circuit:** contain several independent gates in a single package (1 to 10 gates.)
 - ❑ **MS I (Medium Scale Integrated) circuit:** 10 to 200 gates are in a single package. Usually perform specific elementary digital functions such as adders, decoders and registers.

Integrated Circuits (Contd.)

- ▣ **LSI (Large Scale Integrated) circuit:** has 200 to few thousand gates in a single package. They include digital systems such as processors, memory chips and programmable modules.

- ▣ **VLSI (Very Large Scale Integrated) circuit:**
>100,000 gates. Examples : large memory arrays and complex microcomputer chips.
characteristics – size is small and low cost and this is revolutionized the computer system design technology by designing economical computers.

Combinational Circuits

- ❑ A connected arrangement of *logic gates* with a set of inputs and outputs
- ❑ At any given time, the binary values of the outputs are a function of the binary combination of the inputs.
- ❑ This circuits are employed in digital computers for generating binary control decisions and for providing digital components required for data processing.

Combinational Circuits

 


Fig. 4-1 Block Diagram of Combinational Circuit

Designing Combinational Circuits

In general we have to do following steps:

1. Problem description
2. Input/output of the circuit
3. Define truth table
4. Simplification for each output
5. Draw the circuit

Combinational Circuits

- ❑ To demonstrate the design of combinational circuits, two simple arithmetic circuits can be given
 - Half-Adder
 - Full-Adder

- Half-Adder
 - ❑ A combinational circuit that performs the arithmetic addition of two bits is called half adder.

Combinational Circuits


– Half-Adder

- ❑ Input variables of the Half-Adder
 - Augend and addend bits.
- ❑ The Output variables
 - sum and carry
- ❑ It is necessary to specify the two output variables because sum of $1 + 1$ is binary 10. which is two digits.

Exclusive-OR


- ❑ The *XOR* (*exclusive-OR*) gate acts in the same way as the logical "either/or."
- ❑ The output is "true" if either, but not both, of the inputs are "true."
- ❑ The output is "false" if both inputs are "false" or if both inputs are "true."
- ❑ Another way of looking at this circuit is to observe that the output is 1 if the inputs are different, but 0 if the inputs are the same.

Exclusive-OR

 

Truth table for XOR gate		
INPUT		OUTPUT
0	0	0
0	1	1
1	0	1
1	1	0

AND Gate

 


INPUT		OUTPUT	
A	B	$F=A.B$	
0	0	0	False as one or more inputs are false
0	1	0	
1	0	0	
1	1	1	True as all inputs are true

Combinational Circuits: Half Adder

17

- Half Adder : The sum is **XOR** operation and the carry an **AND**

A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

 

$$\text{Sum} = A'B + AB'$$

$$A \oplus B$$


$$\text{Carry} = AB$$

Figure 4-23 (a) Truth table for 1 bit addition. (b) A circuit for a half adder

Combinational Circuits – Full Adder

1. A full adder is a combinational circuit that forms the arithmetic sum of three input bits.
2. It consists three inputs and two outputs.
3. Define a truth table.

Input			Output	
x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 

Combinational Circuits – Full Adder

4. Simplification for each output

Input			Output	
x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$\begin{aligned}
 C &= xy'z + x'yz + xy \\
 &= z(xy' + x'y) + xy \\
 &= z(x \oplus y) + xy
 \end{aligned}$$

$$\begin{aligned}
 S &= xy'z' + x'y'z + xyz + x'yz' \\
 &= z'(xy' + x'y) + z(x'y' + xy) \\
 &= z'(x \oplus y) + z(x \oplus y)' \\
 &= a'b + ab' \quad (\text{let } a=z, b=x \oplus y) \\
 &= x \oplus y \oplus z
 \end{aligned}$$


$$\begin{aligned}
 (x \oplus y)' &= (xy' + x'y)' \\
 &= x'y'' + x''y' \\
 &= x'y + xy' \\
 &= (x' + y)(x + y') \quad \text{Duality} \\
 &= x'x + x'y' + xy + yy' \quad \text{Identity} \\
 &= x'y' + xy
 \end{aligned}$$

Combinational Circuits: Full Adder


20

5. Draw a diagram


Input			Output	
x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 

Maps of Full-Adder

 


$$S = x'y'z + x'yz' + xy'z' + xyz$$

 

$$\begin{aligned} S &= xy + xz + yz \\ &= xy + xy'z + x'yz \end{aligned}$$

Fig. 4-6 Maps for Full Adder

General Digital System Diagram

 

Synchronous and Asynchronous Sequential Logic

□ Synchronous

- the timing of all state transitions is controlled by a common clock
- changes in all variables occur simultaneously

□ Asynchronous


- state transitions occur independently of any clock and normally dependent on the timing of transitions in the input variables
- changes in more than one output do not necessarily occur simultaneously

Synchronous and Asynchronous Sequential Logic (Contd.)

□ Clock

- A clock signal is a square wave of fixed frequency. Often, transitions will occur on one of the edges of clock pulses.
- Clock signals are used to maintain the desired timing in the circuits.
- Clock circuits emit pulse trains of precise repetition interval and width.
- Sometimes it is necessary to have one clock pulse train trail another by a fixed time.
- A circuit with the appropriate delay may be inserted to achieve the desired phase shift.

Clock Signals

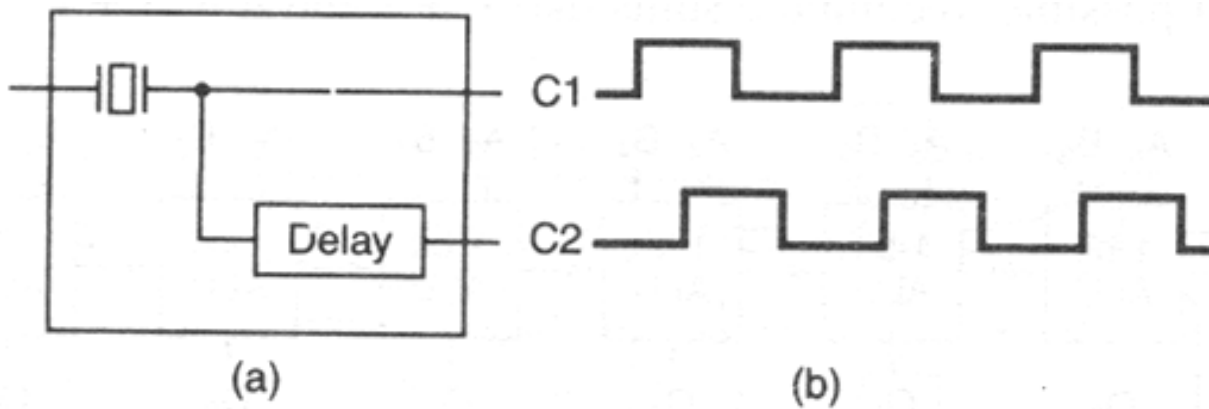

Clock circuit and the clock waveforms

Flip-Flops (Latch)

- ❑ A flip-flop or latch is a circuit that has two stable states and can be used to store state information.
- ❑ This circuit can be made to change state by signals applied to one or more control inputs and will have one or two outputs
- ❑ Flip-flops are the fundamental element of sequential circuits.
 - (gates are the fundamental element for combinational circuits)
- ❑ Flip-flops is a binary cell capable of storing one bit information and basic storage element in sequential logic

Flip-Flops

- ❑ Flip-flops have two outputs
 - One for the normal value (Q)
 - One for the complement value the bit stored it (\overline{Q}).
- ❑ Flip-flops can be either simple (transparent or asynchronous) or clocked (synchronous)
- ❑ the transparent ones are commonly called latches.†
- ❑ The word *latch* is mainly used for storage elements
- ❑ The clocked devices are described as *flip-flops*.


Flip-Flops(Contd.)

- ❑ **Usage:** Flip-flops and latches are a fundamental building block of digital electronics systems used in computers, communications, and many other types of systems.

- ❑ **Main types of flip-flops**
 - S-R(Set-Reset) Flip-Flop
 - D (Data or Delay) Flip Flop
 - J-K Flip-Flop


S-R Flip-Flops

 - A RS-flip-flop is the simplest possible memory element.
- It is constructed by feeding the outputs of two **NOR** gates back to the other **NOR** gates input.



S	R	Action
0	0	Keep state
0	1	$Q=0$
1	0	$Q=1$
1	1	Restricted Combination


S-R Flip-Flops

 

S	R	Action
0	0	Keep state
0	1	$Q=0$
1	0	$Q=1$
1	1	Restricted Combination


- **S=0 and R=0:** Assume the flip flop is set ($Q=0$ and $\overline{Q}=1$), then the output of the top NOR gate remains at $Q=1$ and the bottom NOR gate stays at $\overline{Q}=0$.
- Similarly, when the flip flop is in a reset state ($Q=1$ and $\overline{Q}=0$), it will remain there with this input combination.
- Therefore, with inputs $S=0$ and $R=0$, the flip flop remains in its state.

S-R Flip-Flops

 

- **S=0 and R=1:** Similar to the arguments above, the outputs become $Q=0$ and $\bar{Q}=1$.
- We say that the flip flop is reset.

S-R Flip-Flops

 

S	R	Action
0	0	Keep state
0	1	$Q=0$
1	0	$Q=1$
1	1	Restricted Combination

- **S=0 and R=0:** Assume the flip flop is set ($Q=0$ and $\overline{Q}=1$), then the output of the top NOR gate remains at $Q=1$ and the bottom NOR gate stays at $\overline{Q}'=0$.
- Similarly, when the flipflop is in a reset state ($Q=1$ and $\overline{Q}'=0$), it will remain there with this input combination.
- Therefore, with inputs $S=0$ and $R=0$, the flipflop remains in its state.
- **S=1 and R=1:** This input combination must be avoided.